



الجامعة الألمانية الأردنية
German Jordanian University

Electronics 1 Lab (CME 2410)

School of Informatics & Computing
German Jordanian University

Laboratory Experiment (7)

The Bipolar Junction Transistor (BJT) DC Bias Stabilization

1. Objective:

1. To be familiar with BJT transistors and to learn how they work.
2. To study the concept of biasing a Bipolar Junction Transistor (BJT).

2. Equipment & Instruments

Module No. : DL 3155E14

2 Digital Multimeters

Experiment Part 1 (Common Collector Bias)

1. Components List:

$R_1 = 120\text{ k}\Omega$, $R_2 = 120\text{ k}\Omega$, $R_3 = 6.8\text{ k}\Omega$.

2. Procedure

1) ➔ connect the circuit as shown in Fig. 10.5 ;

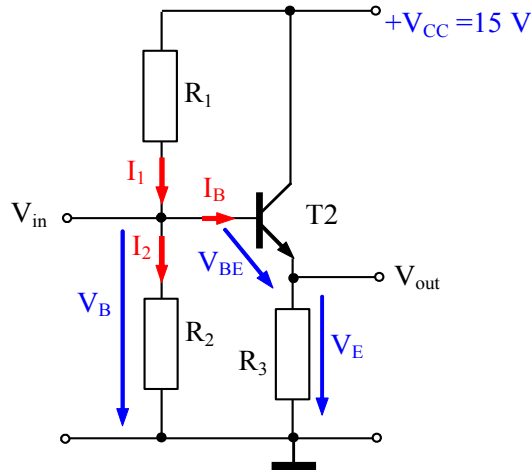


Fig. 10.5: Common collector circuit (emitter follower)

- 2) ➔ measure the voltages V_B , V_E and V_C , determine the emitter current $I_E = \frac{V_E}{R_3}$ by using the measured value of V_E ;
create a Tab. 10.4 (similar to Tab.10.1) and put these value in;
- 3) ➔ calculate the voltages V_B and V_E , considering the voltage $V_{BE} = 0.6\text{V}$;
calculate the value of the emitter current I_E by using the calculated value of V_E ;
put them all as “calculated” values in a second row of Tab. 10.4;
- 4) ➔ measure the voltages between the 3 terminals of the transistor and write these 3 values in a new Tab. 10.5 (similar to Tab.10.2);
- 5) ➔ measure the voltage drops on R_1 and R_2 and write them in further columns of Tab. 10.5 ;
- 6) ➔ calculate the base current I_B and the DC-current gain β_{DC} and write them in further columns of Tab. 10.5 ;
- 7) ➔ observe and comment the carried out measures (transistor currents and bias voltage) and verify that the transistor works in the **active** zone.

Modification insertion

Modification M8

- 1) ➔ remove the cover of the Modifications/Faults simulator and set the eighth dip-switch M8 to ON position (covered dot);
- 2) ➔ measure and record in Tab. 10.6 the collector, base and emitter voltages with reference to ground;
- 3) ➔ **determine if the transistor T2 works:**
 - a. at the saturation point
 - b. in the active region
 - c. at the cut-off point
 - d. at an optimum Q point
- 4) ➔ set the dip-switch M8 back to the initial upwards position;

Modification M9

- 5) ➔ set the dip-switch M9 to ON position (covered dot);
- 6) ➔ measure and record in Tab. 10.6 the collector, base and emitter voltages with reference to ground;
- 7) ➔ **determine if the transistor T2 is:**
 - a. at the saturation point
 - b. at the cut-off point
 - c. in the active region
 - d. with the base-emitter junction in reverse bias;
- 8) ➔ set the dip-switch M9 back to the initial upwards position;

Tab. 10.6

	V_C / V	V_B / V	V_E / V
Modification M8			
Modification M9			

NOTE !!! :

In your conclusions specify what the effect of each modification above is.


Experiment Part 2 (Stability of Fixed Bias Circuit)

1. Components List:

$R1 = 3.3k\Omega$, $R2=470\Omega$, $R3=1M\Omega$, $R4=1k\Omega$, $R5=100\Omega$, $R6=1.5k\Omega$, $R7=390\Omega$,
Heater= 270Ω

2. Procedure

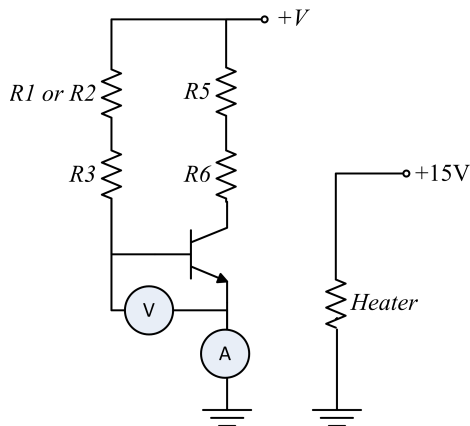- 1) ➡ Connect the circuit as shown with R1 (Make sure to turn R3 completely counter-clockwise – full resistance). **Do not connect the heater to +15V for now.**



- 2) ➡ Adjust the supply voltage +V to 6V
- 3) ➡ Measure the base-emitter voltage and the emitter (collector) current.
- 4) ➡ Connect the heater to +15V and observe the effect of temperature on the fixed bias circuit.
- 5) ➡ After about 5 minutes, record again the base-emitter voltage and the emitter (collector) current.
- 6) ➡ Disconnect the heater and let the transistor cool down.
- 7) ➡ Write down your conclusions related to:
 - Temperature effect on voltages and currents.
 - Temperature effect on bias stability.
- 8) ➡ Repeat previous steps with resistor R2 instead of R1.


Experiment Part 3 (Stability of Voltage Divider Bias)

1. Components List:

$R1 = 3.3k\Omega$, $R2=470\Omega$, $R3=1M\Omega$, $R4=1k\Omega$, $R5=100\Omega$, $R6=1.5k\Omega$, $R7=390\Omega$,
Heater= 270Ω

2. Procedure

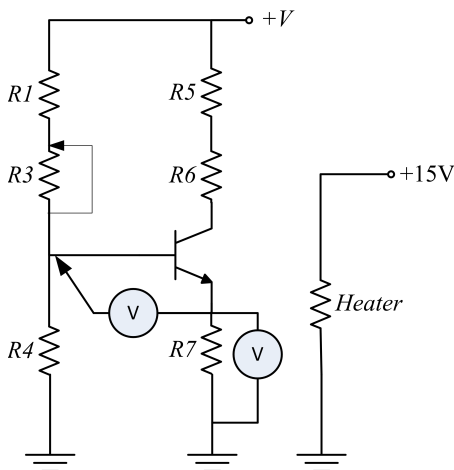- 1) ➔ Connect the circuit as shown with (Make sure to turn R3 completely clockwise – zero resistance). **Do not connect the heater to +15V for now.**



- 2) ➔ Adjust the supply voltage +V to 6V
- 3) ➔ Measure the base-emitter voltage and the emitter voltage. Calculate the collector current.
- 4) ➔ Connect the heater to +15V and observe the effect of temperature on the fixed bias circuit.
- 5) ➔ After about 5 minutes, record again the base-emitter voltage and the emitter voltage and calculate the new collector current.
- 6) ➔ Disconnect the heater.
- 7) ➔ Calculate the stability factors $\Delta I_C\%$ of both types of bias circuits.
- 8) ➔ Write down your conclusions related to:
 - Temperature effect on voltages and currents.
 - Temperature effect on bias stability.
 - Benefit of having the emitter resistor
 - Comparison of stability factors.