



الجامعة الألمانية الأردنية
German Jordanian University

Electronics 1 Lab (CME 2410)

School of Informatics & Computing
German Jordanian University

Laboratory Experiment (8)

The Bipolar Junction Transistor (BJT) AC Amplifier

1. Objective:

1. Verify the operation modalities and the characteristics of various BJT amplifier configurations.
2. Analyze which factors influence the gain.

2. Equipment & Instruments

Module No. : DL 3155E14

2 Digital Multimeters.

Function Generator.

Oscilloscope.


3. Components List:

$R1 = 120k\Omega$, $R2=10k\Omega$, $R4=15k\Omega$, $R5=1k\Omega$, $R6=15k\Omega$, $C1=47\mu F$, $C3=10\mu F$,
 $V1=2N2219A$.

Experiment Part 1 (Using the Kit)


4. Procedure

1) ➡ Connect the circuit as shown:

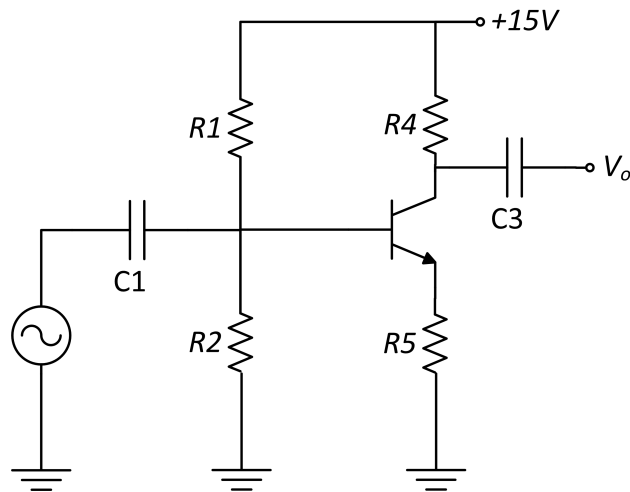

- 2) ➡ Connect an oscilloscope to observe the input to the common-emitter amplifier (base of the transistor) and the output of the amplifier.
- 3) ➡ Adjust the output of the signal generator to a sinusoidal voltage of 1V peak-to-peak, 10kHz at the input of the common-emitter circuit.
- 4) ➡ Observe and draw the output signal. Compare with the input signal.
- 5) ➡ Measure the peak-to-peak output voltage and gain of the amplifier.
- 6) ➡ Connect load resistance R6 to the output and measure the output signal. Compare with the input signal and previous output signal (without R6) in terms of peak-to-peak voltage and gain.

7) ➔ Connect another circuit as shown:

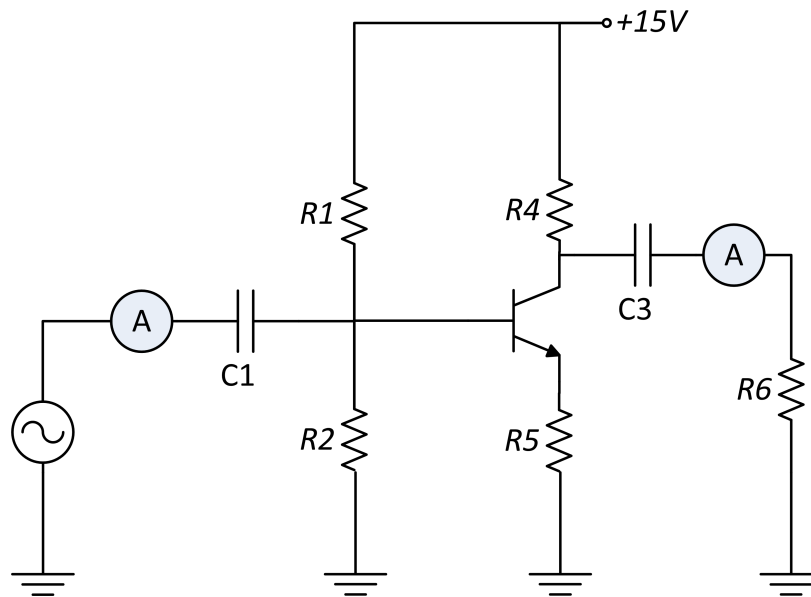

- 8) ➔ Adjust the signal generator to 1V peak-to-peak, 1kHz.
- 9) ➔ Measure the input and output currents and calculate the current gain.
- 10) ➔ Calculate input power and output power from the measured voltages and currents. Then calculate the power gain. Compare this gain with the product of the power and current gains.
- 11) ➔ Reconnect the 1st circuit with load resistance R6, and signal generator at 1kHz.
- 12) ➔ Measure with a multimeter the voltage across R2. Divide this by the measure input current to obtain the input resistance of the amplifier. Compare this with the calculated value $R_{in} = (r'_b + \beta R5) \parallel R1 \parallel R2$ where $\beta = 100$, $r'_b = 5.1k\Omega$
- 13) ➔ Calculate the gain as:

$$A_v = \frac{R4 \parallel R6}{R5 + r'_b / \beta}$$

- 14) ➔ Compare with the measured value
- 15) ➔ Calculate the measure output resistance as:

$$R_{out} = \frac{V_{o(withoutR6)} - V_{o(withR6)}}{V_{o(withR6)}} \cdot R6$$

Explain how this equation is derived and compare result with calculated $R_{out}=R4$

Modification M1 (Changes R1 from 120k to 10k)

- 16) ➔ Adjust the output of the function generator to 1Vpp, 10kHz.
- 17) ➔ Set the 1st dipswitch M1 to ON position (covered dot) and observe the output.
- 18) ➔ Increase the amplitude of the input signal and observe the output. Explain what is happening.

19) ➡ Set M1 back to the OFF position.

Modification M2 (Changes R4 from 15k to 2.7k)

20) ➡ Set the amplitude of the input signal to 1Vpp.

21) ➡ Set the 2nd dipswitch M2 to ON position (covered dot) and observe the output.

22) ➡ Remove and put again the load R6 and observe the output.

23) ➡ Set M2 back to the OFF position.

Modification M3 (Changes R2 from 10k to 3.3k)

24) ➡ Set the 3rd dipswitch M3 to ON position (covered dot) and observe the output.

25) ➡ Observe the signal at the various test points in the circuit.

26) ➡ Set M3 back to the OFF position.

Experiment Part 2 (Using the breadboard)

1. Design a common emitter amplifier with a gain of 20.
2. Build it using the individual components on the breadboard.
3. insert an input signal and measure the output to check your amplifier.